



MADE EASY

India's Best Institute for IES, GATE & PSUs

Memory Based Questions of GATE 2020 Electrical Engineering

Detailed Solutions

**Date of Exam : 8/2/2020
Forenoon Session**

Scroll down to view

www.madeeasy.in

Corporate Office: 44-A/1, Kalu Sarai, New Delhi - 110016 | **Ph:** 011-45124612, 9958995830

Delhi | Hyderabad | Noida | Bhopal | Jaipur | Lucknow | Indore | Pune | Bhubaneswar | Kolkata | Patna

- Q.1** NPA is the asset that a customer borrows and holds it for a period of time without paying any interest. RBI has reduced the holding period for NPA thrice during the period 1993-2004. In 1993 it was four quarters (360 days) how many days is the holding period in 2004?
- (a) 90 (b) 180
(c) 45 (d) 270

Ans. (a)


End of Solution

- Q.2** Number between 1001 to 9999 how many times 37 occurs in same sequence?
- (a) 279 (b) 280
(c) 270 (d) 299

Ans. (a)

End of Solution

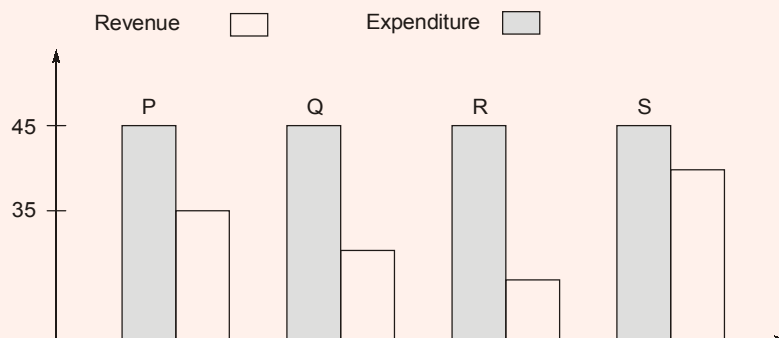- Q.3** The revenue and expenditure of four companies P, Q, R, S as shown in the figure below company Q earns a profit of 10% on expenditure of 2014, the revenue of Q in 2015 is _____.



Ans. ()
Data insufficient

End of Solution

- Q.4** Stock markets _____ at the news of the coup.
- (a) plugged (b) plunged
(c) probed (d) poised

Ans. (b)

End of Solution

Q.5 This book, including all its chapters, _____ interesting. The students as well as instructor _____ in agreement with it.

- (a) is, was (b) is, are
(c) were, was (d) are, are

Ans. (b)

End of Solution

Q.6 People were prohibited _____ there vehicles near the entrance of the main administrative building.

- (a) to park (b) to have parked
(c) from parking (d) parking

Ans. (c)

End of Solution


Q.7 Select the word do : undo : : trust :

- (a) distrust (b) entrust
(c) intrust (d) untrust

Ans. (a)

End of Solution

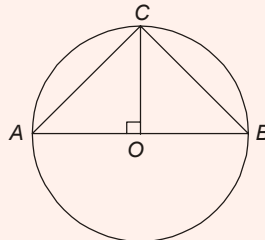Q.8 Find the ratio of $\frac{\overline{AC} + \overline{BC}}{\overline{AB}}$ where O is center of the circle shown below.



\overline{AB} , \overline{AC} and \overline{BC} are chords.

Ans. (1.414)

End of Solution

Q.9 Z : WV : RQP : ?

- (a) KIJH (b) JIHG
(c) HIJK (d) KJIH

Ans. (d)

End of Solution

Q.10 If P, Q, R, S are four individual, how many team of size exceeding one can be formed with Q as a member?

- (a) 5 (b) 7
(c) 8 (d) 6

Ans. (b)

End of Solution

Q.11 A resistor and a capacitor are connected in series to a 10 V dc supply through a switch is closed at $t = 0$, and the capacitor voltage is found to cross '0' voltage at $t = 0.4\tau$ (τ = time constant). The absolute value of % change required in the initial capacitor voltage if the zero crossing has to happen at $t = 0.2\tau$ is ____.

Ans. (54.989)

If initial charge polarities on the capacitor is opposite to the supply voltage then only the capacitor voltage crosses the zero line.

$$V_c(t) \Rightarrow \text{Final value} + (\text{Initial value} - \text{Final value}) e^{-t/\tau}$$

$$0 = 10 + (-V_0 - 10) e^{-0.4}$$

$$10 = (V_0 + 10) e^{-0.4}$$

$$V_0 = 4.918 \text{ V}$$


Now,

$$t = 0.2\tau$$

$$0 = 10 + (-V'_0 - 10) e^{-0.2}$$


$$V'_0 = 2.214$$
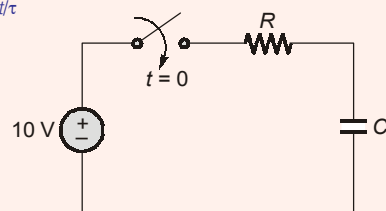
$$\% \text{change in voltage} = \frac{4.918 - 2.214}{4.918} \times 100\% = 54.989\%$$



End of Solution

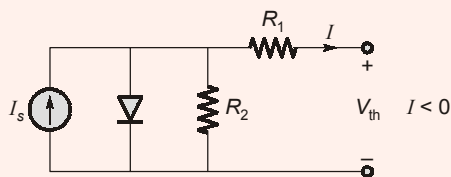Q.12 To ensure the maximum power transfer across V_{th} the values of R_1 and R_2 will be (Diode in figure is silicon diode)




- (a) R_1 high, R_2 high (b) R_1 low, R_2 low
(c) R_1 low, R_2 high (d) R_1 high, R_2 low


Ans. (b)

End of Solution

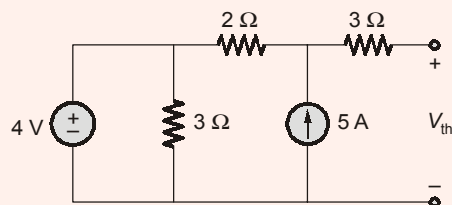Q.13 For the given circuit the value of V_{th} is _____.



Ans. (14)

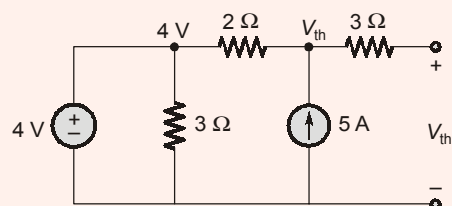


$$\frac{V_{th} - 4}{2} = 5$$

$$V_{th} = 14 \text{ V}$$

End of Solution

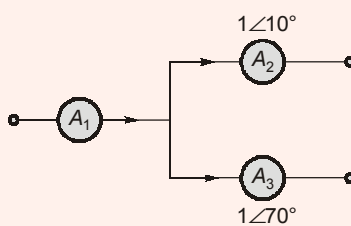Q.14 In the given circuit rms value of I_1 is _____.



Ans. (1.732)

From KCL,

$$I_1 = 1\angle 10^\circ + 1\angle 70^\circ$$

$$I_1 = 1.732\angle 40^\circ$$

End of Solution

Q.15 If 2001 → 98H
 2002 → B1H
 LXI H, 2001H
MVI A, 21H
INX H
ADD M
INX H
MOV M, A
HLT
The content of 2003H is (____)₁₆.

Ans. (210)

LXI H, 2001 H \rightarrow

H	L
20	01

MVI A, 21 H → A
21H

INX H \rightarrow HL + 1

H	L
20	02

ADD M → [A] + data @ reference of HL pair

$$21 \text{ H} + \text{B1H} = \text{D2H} \rightarrow [\text{A}]$$
$$\text{INX} \quad \text{H} \quad \rightarrow [\text{HL}] + 1 \rightarrow 2002\text{H} + 1\text{H} \rightarrow 2003\text{H}$$

MOV M, A → [A] to Memory, i.e., @ reference of HL pair

2003H $\boxed{D2} \leftarrow \overset{A}{\boxed{D2}}$

HLT → Stop

∴ content in the 2003 H is D2H

Converting in decimal

$$D \times 16^1 + 2 \times 16^0 \Rightarrow 13 \times 16 + 2 = (210)_{10}$$

End of Solution

Q.16 A differential equation with $y(t) \rightarrow$ output and $x(t) \rightarrow$ input is

$$\frac{d^2 y(t)}{dx^2} + 4y(t) = 6x(t)$$

The poles of the input

- (a) $-2j, +2j$ (b) $+4, -4$
(c) $-2, +2$ (d) $+4j, -4j$

Ans. (a)

$$\frac{d^2 y(t)}{dt^2} + 4y(t) = 6x(t)$$

Taking Laplace transform,

$$s^2 Y(s) + 4Y(s) = 6X(s)$$

$$\frac{Y(s)}{X(s)} = \frac{6}{s^2 + 4}$$

∴ Poles are at $s^2 + 4 = 0$

$$\Rightarrow s = \pm 2j$$

End of Solution

Q.17 A PMDC motor is connected to 5 V at $t = 0$. Its speed increases from 0 to 6.32 rad/sec monotonically from $t = 0$ to $t = 0.5$ s and finally settles down to 10 rad/sec. Assume negligible armature inductance. Find the transfer function?

(a) $\frac{10}{1+0.5s}$

(b) $\frac{10}{s+0.5}$

(c) $\frac{2}{1+0.5s}$

(d) $\frac{2}{s+0.5}$

Ans. (c)

6.32 is 63% of 10.

∴ $t = 0.5$ s is nothing but time constant

Also, output is double of input.

∴ DC gain of system is 2.

Hence, option (c) is correct.

Alternative Solution :

When the armature inductance is neglected the transfer function of PMDC motor becomes,

$$\frac{\omega_m(s)}{V_a(s)} = \frac{k_m}{1+sT_m} \quad \dots(i)$$

$$\Rightarrow \omega_m(s) = V_a(s) \cdot \frac{k_m}{1+sT_m}$$

As input is 5 V i.e. $V_a(s) = \frac{5}{s}$

$$\therefore \omega_m(s) = \frac{5 k_m}{s(1+sT_m)} \quad \dots(ii)$$

As the final value of $\omega_m = 10$ rad/sec

Using final value theorem,

$$\lim_{s \rightarrow 0} s \omega_m(s) = \lim_{s \rightarrow 0} s \frac{5 k_m}{s(1+sT_m)} = 10$$

$$\Rightarrow k_m = 2$$

$$\text{From (ii) equation, } \omega_m(s) = \frac{10}{s(1+sT_m)} = \frac{a_0}{s} + \frac{a_1}{1+sT_m}$$

$$\omega_m(s) = \frac{10}{s} - \frac{10T_m}{1+sT_m}$$

ESE 2020 Main Exam

Streams: **CE** **ME** **EE** **E&T**



MADE EASY
India's Best Institute for IES, GATE & PSUs

Classroom Course

Batches from
18th Feb, 2020

Conventional Questions Practice Programme

Location : Delhi Centre

- 300-350 Hrs of comprehensive classes.
- Dynamic test series in synchronization with classes.
- Well designed comprehensive Mains workbooks.
- Special sessions to improve writing skills, time management & presentation skills.

Admission open

Online Classes

Batches from
25th Feb, 2020

Conventional Questions Practice Programme

- 300-350 Hrs of comprehensive recorded sessions.
- Convenience of learning at your own pace.
- Physical study materials will be provided at your address.

Admission open

Mains Test Series

Batches from
15th Mar, 2020

15 Tests | Mode : Offline/Online

- Test series will be conducted in synchronisation with subjects taught in the classes.
- Exactly on the UPSC pattern and standard.
- Contains **Repeat Topics** and **New Topics** to maintain continuity in study.
- Facility to cross check the evaluated answer sheet & access to the top scorer copy.
- Time bound evaluation of answer sheets with feedback.

Admission open

$$\omega_m(t) = 10 - 10^{-t/T_m}$$

It is given that at $t = 0.5$ sec,

$$\omega_m = 6.32 \text{ rad/sec}$$

$$\therefore 6.32 = 10 - 10e^{-0.5/T_m}$$

$$\Rightarrow e^{-0.5/T_m} = 0.368$$

$$\frac{-0.5}{T_m} = \ln(0.368)$$

$$\frac{-1}{2T_m} = -0.999$$

$$T_m = \frac{1}{1.999} \simeq \frac{1}{2} = 0.5$$

Substituting the value of k_m and T_m in T.F. in equation (i)

$$\frac{\omega_m(s)}{V_a(s)} = \frac{2}{1 + 0.5s}$$

End of Solution

- Q.18** For the given open loop transfer function $\frac{K}{(s+a)(s-b)(s+c)}$. If $1 + G(s)H(s)$ plane encircles the origin once in counter clockwise direction then number of closed loop poles in right side of s-plane will be

Ans. (0)

$$N_+ = P_+ - Z_+$$

$$N_+ = +1 \text{ (as CCW direction)}$$

$$P_+ = 1$$

$$\therefore Z_+ = P_+ - N_+ \\ = 1 - 1 = 0$$

End of Solution

- Q.19** For the given open loop transfer function with unity negative feed back gain,

$$G(s)H(s) = \frac{s^2 + s + 1}{s^3 + 2s^2 + 2s + K}$$

The value of gain K . For which closed loop system is marginally stable will be _____

Ans. (8)

$$\text{CE is } 1 + G(s)H(s) = 0$$

$$\Rightarrow 1 + \frac{s^2 + s + 1}{s^3 + 2s^2 + 2s + K} = 0$$

$$\Rightarrow s^3 + 3s^2 + 3s + (1 + K) = 0$$

R.H. criteria

$$\begin{array}{c|cc} s^3 & 1 & 3 \\ s^2 & 3 & (1+K) \\ s^1 & 9-(1+K) & 0 \end{array}$$

for marginal stability

$$9 - (1 + K) = 0$$

$$\Rightarrow K = 8$$

End of Solution

Q.20 A stable LTI system with single pole P , has a transfer function $G(s)H(s) = \frac{s^2 + 100}{s - P}$ with

DC gain of 5; the smallest possible frequency in radian/sec at only gain is

- (a) 11.08 (b) 70.13
(c) 122.07 (d) 8.84

Ans. (d)

$$G(s)H(s) = \frac{s^2 + 100}{s - p}$$

Given, $K = 5$

$$\frac{s^2 + 100}{-P\left(1 - \frac{S}{P}\right)} = 100 \frac{\left(1 + \frac{s^2}{100}\right)}{-P\left(1 - \frac{s}{P}\right)}$$

$$\text{DC gain} = -\frac{100}{P} = 5$$

$$\Rightarrow P = -20$$

$$\therefore G(s)H(s) = \frac{s^2 + 100}{s + 20}$$


$$G(j\omega)H(j\omega) = \frac{100 - \omega^2}{20 + j\omega}$$

$$|G(j\omega)H(j\omega)| = \frac{100 - \omega^2}{\sqrt{20^2 + \omega^2}} = 1$$

$$\Rightarrow \omega = 8.84 \text{ rad/sec}$$

End of Solution

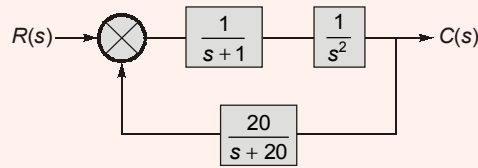
Q.21 For the given block diagram of the system



which of the following is true regarding order and stability of the system

- (a) 4th order and stable (b) 4th order and unstable
(c) 3rd order and unstable (d) 3rd order and stable

Ans. (b)

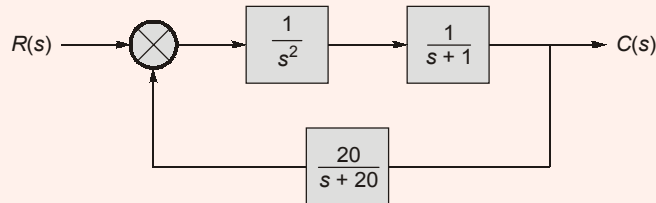

CE is $1 + G(s) H(s) = 0$

$$1 + \frac{1}{s^2(s+1)} \times \frac{20}{(s+20)} = 0$$

$$\Rightarrow (s^3 + s^2)(s+20) + 20 = 0$$


$$s^4 + 21s^3 + 20s^2 + 20 = 0$$

$$s^4 + 21s^3 + 20s^2 + 20 = 0$$

As coefficient of s' is missing system is of 4th order and unstable.

End of Solution

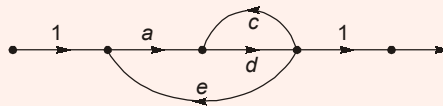Q.22 Which of the given below signal flow is analogous to given below system?



Ans. ()

End of Solution

Q.23 Given $\vec{D} = 15\hat{a}_p + 2P\hat{a}_\phi - 3Pz\hat{a}_z \left(\frac{C}{m^2} \right)$, find electric flux crossing the cylinder $\rho = 3$ m;

3 varying from 0 to 5.

Ans. (180 π)

$$\Psi / \text{Crossing closed surface} = \oint \vec{D} \cdot d\vec{s} = \iiint (\nabla \cdot \vec{D}) dv \quad \dots(i)$$

$$\nabla \cdot \vec{D} = \frac{1}{\rho} \frac{\partial}{\partial \rho} (\rho D_\rho) + \frac{1}{\rho} \frac{\partial D_\phi}{\partial \phi} + \frac{\partial D_z}{\partial z}$$

$$\begin{aligned}
 &= \frac{1}{\rho} \frac{\partial}{\partial \rho} (\rho 15) + \frac{1}{\rho} \frac{\partial}{\partial \phi} (2\rho) + \frac{\partial}{\partial z} (-3\rho z) = \frac{1}{\rho} 15 - 3\rho \\
 \iiint (\vec{\nabla} \cdot \vec{D}) dv &= \iiint \left(\frac{15}{\rho} - 3\rho \right) \rho d\rho d\phi dz \\
 &= \iiint 15 d\rho d\phi dz - 3 \iiint \rho^2 d\rho d\phi dz \\
 &= 15 \int_{\rho=0}^3 d\rho \int_{\phi=0}^{2\pi} d\phi \int_{z=0}^5 dz - 3 \int_{\rho=0}^3 \rho^2 d\rho \int_{\phi=0}^{2\pi} d\phi \int_{z=0}^5 dz \\
 &= 15(3-0)(2\pi)(5) - 3 \left(\frac{3^3}{3} \right) (\pi)(5) \\
 &= 45(10\pi) - 27(10\pi) = 180\pi = 565.2 \text{ C}
 \end{aligned}$$

End of Solution

Q.24 The vector function expressed by

$$\vec{F} = a_x(5y - k_1 z) + a_y(3z + k_2 x) + a_z(k_3 y - 4x)$$

represent a conservative field, where a_x, a_y, a_z are unit vector along x, y, z directions, respectively the value of constant k_1, k_2 and k_3 _____.

- (a) 4, 5, 3 (b) 8, 3, 7
(c) 0, 0, 0 (d) 3, 8, 5

Ans. (a)

$$\vec{F} = (5y - k_1 z)\hat{i} + (3z + k_2 x)\hat{j} + (k_3 y - 4x)\hat{k}$$

is conservative field

$$\vec{F} \text{ is irrotational, } \nabla \times \vec{F} = 0$$


$$\begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ 5y - k_1 z & 3z + k_2 x & k_3 y - 4x \end{vmatrix} = 0$$

$$\hat{i}(k_3 - 3) - \hat{j}(-4 + k_1) + \hat{k}(k_2 - 5) = 0$$

$$\begin{array}{lll}
 k_3 - 3 = 0 & 4 - k_1 = 0 & k_2 - 5 = 0 \\
 k_3 = 3 & k_1 = 4 & k_2 = 5 \\
 k_1 = 4 & k_2 = 5 & k_3 = 3
 \end{array}$$

End of Solution

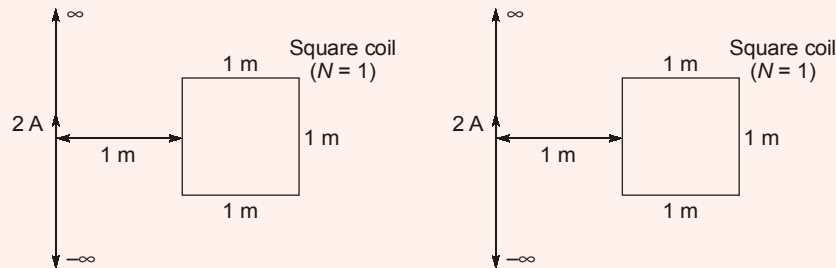Q.25 The value of mutual inductance figure shows long wire carrying current 2 A placed in away from square coil as shown in figure. The value mutual inductance will be ____ nH.



Ans. (138.6)

$$\phi \propto I$$

$$\phi = MI$$

$$\vec{B} = \frac{\mu_0 I}{2\pi\rho} \hat{a}_\phi \quad (\vec{B} \text{ due to infinite long line})$$

Magnetic flux crossing square loop is

$$\phi = \iint \vec{B} \cdot d\vec{s}$$

$$= \iint \frac{\mu_0 I}{2\pi\rho} \hat{a}_\phi \cdot (d\rho dz) \hat{a}_\phi = \frac{\mu_0 I}{2\pi} \int_{\rho=1}^2 \frac{d\rho}{\rho} \int_{z=0}^1 dz$$

$$\phi = \frac{\mu_0 I}{2\pi} (\ln \rho)_{\rho=1}^2 (z)_{z=0}^1$$

$$\phi = \frac{\mu_0 I}{2\pi} (\ln 2)$$

$$m = \frac{\phi}{I}$$

$$m = \frac{\mu_0 (\ln 2)}{2\pi} = \frac{4\pi \times 10^{-7} (\ln 2)}{2\pi}$$

$$m = 1.386 \times 10^{-7} \text{ Henry}$$

End of Solution

Q.26 In a dielectric medium $\epsilon_r = 2.25$ and $\vec{E} = 2r \hat{a}_r + \frac{3}{r} \hat{a}_\phi + 6\hat{a}_z$ in cylindrical, then find volume charge density

(a) $2\epsilon_0$

(b) $3\epsilon_0$

(c) $4\epsilon_0$

(d) $9\epsilon_0$

Ans. (d)

$$\vec{D} = \epsilon \vec{E} = \epsilon_0 \epsilon_r \vec{E}$$

$$\vec{D} = \epsilon_0 2.25 \left(2r \hat{a}_r + \frac{3}{r} \hat{a}_\phi + 6\hat{a}_z \right)$$

$$\vec{D} = 4.5\epsilon_0 r \hat{a}_r + \frac{6.75\epsilon_0}{r} \hat{a}_\phi + 13.5\epsilon_0 \hat{a}_z$$

Volume charge density


$$\rho_v = \vec{\nabla} \cdot \vec{D}$$

$$\rho_v = \frac{1}{r} \frac{\partial}{\partial r} (rD_r) + \frac{1}{r} \frac{\partial D_\phi}{\partial \phi} + \frac{\partial D_z}{\partial z}$$

$$\begin{aligned} \rho_v &= \frac{1}{r} \frac{\partial}{\partial r} (r \cdot 4.5\epsilon_0 r) + \frac{1}{r} \frac{\partial}{\partial \phi} \left(\frac{6.75\epsilon_0}{r} \right) + \frac{\partial}{\partial z} (13.5\epsilon_0) \\ &= \frac{1}{r} \frac{\partial}{\partial r} (4.5\epsilon_0 r^2) + 0 + 0 \\ &= \frac{1}{r} (4.5\epsilon_0) (2r) = 9\epsilon_0 \end{aligned}$$

End of Solution

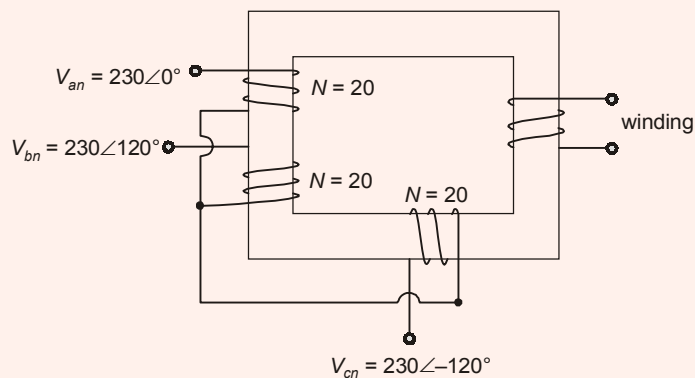- Q.27** In the given figure, the three windings having polarity as shown above, are connected to 3- ϕ , balanced supply. The number of turns in the supply winding is 20, the voltage seen in winding X having $N = 2$ turns will be



Ans. (46)

$$\begin{aligned} V_4 &= \frac{2}{20} (230\angle 0^\circ - 230\angle 120^\circ - 230\angle -120^\circ) \\ &= 46\angle 0^\circ \text{ V} \end{aligned}$$

End of Solution

- Q.28** A cylindrical rotor synchronous generator delivering constant active power at a constant terminal voltage, a current of 100 A at a 0.9 p.f. lagging. A shunt reactor is connected so that the reactive power demand doubles then the new value of armature current is _____ A.

Ans. (125.29)

$$\begin{aligned} \text{At } P_{\text{constant}}, \quad I_{a1} \cos \phi_1 &= I_{a2} \cos \phi_2 \\ \cos \phi_1 &= 0.9 \end{aligned}$$

$$\begin{aligned}\tan \phi_1 &= 0.484 = \frac{Q}{P} \\ \Rightarrow \frac{2Q}{P} &= 0.9686 = \tan \phi_2 \\ \cos \phi_2 &= 0.7182 \\ \therefore 100 \times 0.9 &= I_{a2} \times 0.7182 \\ \Rightarrow I_{a2} &= 125.29 \text{ A}\end{aligned}$$

End of Solution

Q.29 A cylindrical rotor generator having internal emf $1 + j0.7$ V and terminal voltages $(1 + j0.0)$ V. The synchronous reactance is 0.7 pu whereas subtransient reactance is 0.2 pu for 3- ϕ bolted short circuit at generator the value of subtransient generated internal emf is _____.

Ans. (1.019)

$$\text{Prefault current, } I_0 = \frac{E_f - V_t}{jX_d} = \frac{1 + j0.7 - 1}{j0.7} = 1$$

Subtransient induced emf,

$$E_f'' = V_0 + jX_d'' I_0 = 1 + j0.2 \times 1 = 1 + j0.2$$

End of Solution

Q.30 4 kVA, 200/100 V, 50 Hz single phase transformer has no load core loss of 450 W. If high voltage side is energized by 160 V, 40 Hz, the core loss will be 320 W. Find the core loss if the high voltage side is energized by 100 V, 25 Hz.

Ans. (162.5)

$$200 \text{ V, } 50 \text{ Hz, } P_c = 450 \text{ Watt}$$

$$160 \text{ V, } 40 \text{ Hz, } P_c = 320 \text{ Watt}$$

$$100 \text{ V, } 25 \text{ Hz, } P_c = ? \text{ Watt}$$

$$\frac{V}{f} = \text{const.} = \frac{200}{50} = \frac{160}{40} = \frac{100}{25}$$

So,

$$P_c = Af + Bf^2$$

$$450 = A \times (50) + B \times (50)^2 \quad \dots(i)$$

$$320 = A \times (40) + B \times (40)^2 \quad \dots(ii)$$

From (i) and (ii),

$$\frac{450}{50} = A + B(50) \quad \dots(iii)$$

$$\frac{320}{40} = A + B(40) \quad \dots(iv)$$

(iii) - (iv),

$$(9 - 8) = B(10)$$

$$B = \frac{1}{10}$$

and $A = 9 - \frac{1}{10} \times 50$
 $A = 4$

Now at 100 V, 25 Hz,

$$P_c = 4 \times 25 + \frac{1}{10} \times (25)^2$$

$$= 100 + 62.5 = 162.5 \text{ Watt}$$

End of Solution

Q.31 A 3- ϕ , 50 Hz, 4 pole induction motor runs at no load with a slip of 1%, at full load the motor runs at a slip of 5%. The percentage speed regulation of the motor is ____.

Ans. (4.02)

4 pole, 50 Hz I.M has no load slip 1%

4 pole, 50 Hz I.M has full load slip 5%

$$N_s = 1500 \text{ rpm}$$

$$N_0 = N_s(1 - s) = 1500(1 - 0.01) = 1485$$

$$N = N_s(1 - s) = 1500(1 - 0.05) = 1425$$

Speed regulation is

$$\%S.R. = \frac{N_0 - N}{N} \times 100 = \frac{1485 - 1425}{1425} \times 100 = 4.02\%$$

End of Solution

Q.32 A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequence detectable. For the sequence (1, 0, 1) and input data (1, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 1, 0) the output is

Ans. ()

End of Solution

Q.33 A synchronous generator has lossless reactance X_s . Then V_A is terminal voltage and E_f is internal emf voltage.

P : If power factor is leading then always $V_A > E_f$

Q : If power factor is lagging then always $V_A < E_f$

Which of the statement is true?

(a) P is false, Q is true

(b) P is false, Q is false

(c) P is true, Q is true

(d) P is true, Q is false

Ans. (a)

End of Solution

- Q.34** A 250 V DC shunt motor having armature resistance of 0.2Ω and field resistance of 100Ω . It draws a no load current of 5 A at 1200 rpm . The brush drop is 1 V per brush at all operating conditions. If motor draws 50 A at full load and flux per pole is decreased by 5% because of armature reaction. The speed of the motor at full load is ____ rpm.
- (a) 900 (b) 1000
(c) 1200 (d) 1220

Ans. (d)

No load current 5 A

B.R.D = 1 V per brush

loaded, $I_L = 50 \text{ A}$

$$R_{sh} = 100 \Omega$$

$$I_{sh} = \frac{250}{100} = 2.5 \text{ A}$$

$$I_{a0} = 2.5 \text{ A}$$

$$I_{aL} = 47.5 \text{ A}$$

$$V = E_b + I_a R_a + \text{B.R.D}$$


$$\begin{aligned} E_{b \text{ no load}} &= V - I_{a0} R_a - \text{B.R.D} \\ &= 250 - 2.5(0.2) - 1 \times 2 \\ &= 247.5 \text{ Volts} \end{aligned}$$

$$\begin{aligned} E_{b \text{ load}} &= 250 - 47.5(0.2) - 1 \times 2 \\ &= 238.5 \text{ volts} \end{aligned}$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$


$$\frac{N_2}{1200} = \frac{238.5}{247.5} \times \frac{\phi_1}{0.95\phi_1}$$

$$N_2 = 1217.22 \text{ rpm}$$

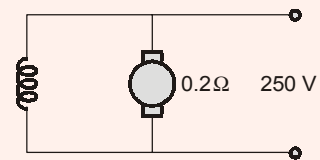

End of Solution

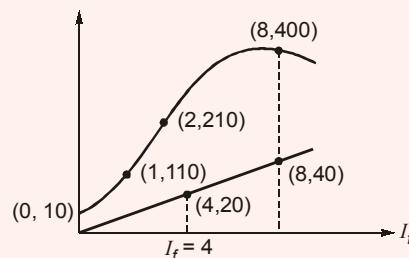- Q.35** Find $\frac{Z_{(\text{unsaturated})}}{Z_{(\text{saturated})}} = ?$




Ans. (2.05)

$$X_{s \text{ unsat}} = \frac{410}{20} = 20.5 \text{ V}$$

$$X_{s \text{ sat}} = \frac{400}{40} = 10 \text{ } \Omega$$

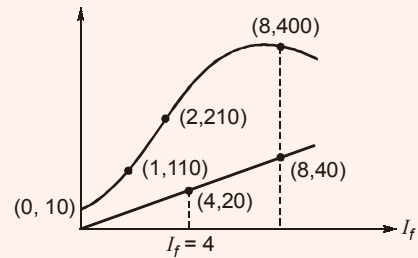
$$\Rightarrow \frac{X_{s \text{ unsat}}}{X_{s \text{ sat}}} = 2.05$$



(Data may not be accurate as it is a memory based graphical question.)

End of Solution

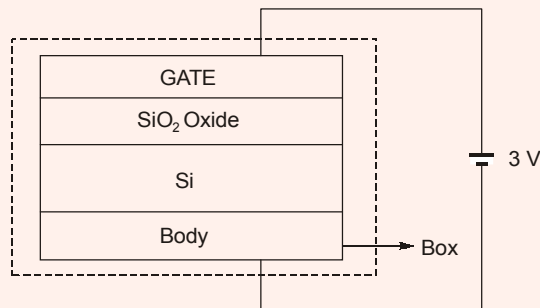Q.36 DC bias voltage of 13 V is applied between gate and body time. The charge measured in the silicon dioxide layer is +Q,



The total charge in the box region is _____ multiple of +Q. (Give answer to nearest integer)

Ans. (#)
A

End of Solution

Q.37 A diode is biased of -0.03 V having an ideality factor of $\frac{15}{13}$; and $V_T = 26 \text{ mV}$; if the current has to be raised to 1.5 times of the than required voltage will be
(a) -4.5 V (b) -0.09 V
(c) -0.02 V (d) None of above

Ans. (c)

Given data: $V_{D1} = 0.03 \text{ V} = -30 \text{ mV}$

$$\eta = \frac{15}{13}; \quad V_T = 26 \text{ mV}$$

$$I_{D2} = 1.5 I_{D1}$$

$$I_{D2} = I_s e^{V_{D2}/\eta V_T} \quad \dots(i)$$

$$I_{D1} = I_s e^{V_{D1}/\eta V_T} \quad \dots(ii)$$

**New
Batches**



MADE EASY
India's Best Institute for IES, GATE & PSUs

ESE 2021 GATE 2021

1 Year/2 Years
Classroom Courses

Regular

Weekend

Early Start... • Extra Edge...

BATCH COMMENCEMENT DATES

Delhi and Noida

REGULAR BATCHES

DELHI Evening :

ME : 16th Jan, 2020
25th Feb, 2020
CE : 30th Jan, 2020
20th Feb, 2020
EE, EC : 20th Jan, 2020

Morning :
CE, ME : 12th Feb, 2020
(Batch Closed)

EE : 18th Feb, 2020
EC : 6th Apr, 2020
CS : 18th May, 2020

WEEKEND BATCHES

DELHI

CE : 1st Feb, 2020
ME : 9th Feb, 2020
EE : 22nd Feb, 2020
EC : 22nd Feb, 2020

NOIDA

CE & ME : 8th Feb, 2020
EC & EE : 18th Jan, 2020
16th Feb, 2020

Rest of India

Patna : 24-02-2020

Lucknow : 20-02-2020

Bhopal : 16-01-2020

Indore : 20-02-2020

Pune : 10-02-2020

Hyderabad : 16-03-2020

Bhubaneswar : 23-01-2020

Kolkata : 25-01-2020

Jaipur : 16-02-2020

Equation (i) and (ii),

$$\frac{I_{D2}}{I_{D1}} = e^{(V_{D2} - V_{D1}) / \eta V_T}$$

$$V_{D2} - V_{D1} = \eta V_T \ln \left(\frac{I_{D2}}{I_{D1}} \right)$$

$$= \frac{15}{13} \times 26 \text{ mV} \ln \left(\frac{1.5 I_{D1}}{I_{D1}} \right)$$

$$= 15 \times 2 \text{ mV} \ln (1.5)$$

$$= 30 \text{ mV} \times 0.40 = 12 \text{ mV}$$

$$V_{D2} - (-30 \text{ mV}) = 12 \text{ mV}$$

$$V_{D2} = 12 \text{ mV} - 30 \text{ mV}$$

$$= -18 \text{ mV} = -0.018 \text{ V}$$

End of Solution

Q.38 For a common source amplifier $g_m = 520 \mu\text{A/V}^2$ and $r_d = 4.7 \text{ k}\Omega$ calculate gain of amplifier.

(a) -2.447

(b)

(c)

(d)

Ans. (a)

$$g_m = 520 \mu\text{A/V}^2$$

$$r_d = 4.7 \text{ k}\Omega$$

$$A_v = -g_m r_d$$

$$= -520 \mu\text{A/V}^2 \times 4.7 \text{ k}\Omega$$

$$= -2.447$$

End of Solution

Q.39 A causal control system having poles at $(-2, 1)$, $(2, -1)$ and zeros at $(2, 1)$ and $(-2, -1)$. Identify the nature of transfer function.

(a) Unstable, complex, all pass

(b) Stable, real, all pass

(c) Unstable, complex, HP

(d) Stable, real, HPF

Ans. (a)

All pass filter because poles and zeros are mirror-image of each other (i.e. for each pole there is a mirror-image zero).


Unstable because one pole in the RHS of s-plane.

\Rightarrow

$$H(s) = \frac{[s - (-2 + j)][s - (2 - j)]}{s - (2 + j)][s - (-2 - j)]}$$

$$= \frac{[s + (2 - j)][s - (2 - j)]}{[s - (2 + j)][s + (2 + j)]}$$
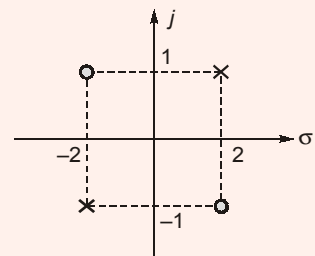
$$= \frac{s^2 - (2 - j)^2}{s^2 - (2 + j)^2} = \frac{s^2 - [4 - 1 - 4j]}{s^2 - [4 - 1 + 4j]} = \frac{s^2 - (3 - 4j)}{s^2 - (3 + 4j)}$$



Transfer function is complex.

$h(t)$ or impulse response will be also complex because poles are not occurring in conjugate pair as well as zeros are also not occurring in conjugate pair.

End of Solution

Q.40 $x(t) * h(t) = y(t)$, where $h(t)$ is impulse response.

$|x(t)| * |h(t)| = z(t)$ then which of the following is correct.

- (a) For every $-\infty < t < \infty$, $z(t) \leq y(t)$ (b) For every $-\infty < t \leq \infty$, $z(t) \geq y(t)$
(c) For some $-\infty < t < \infty$, $z(t) \leq y(t)$ (d) For some $-\infty < t \leq \infty$, $z(t) \geq y(t)$

Ans. (b)


Since,

$$y(t) = x(t) + h(t)$$

and

$$z(t) = |x(t)| * |h(t)|$$


Case-1:

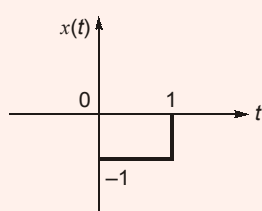



then,

$y(t)$


and

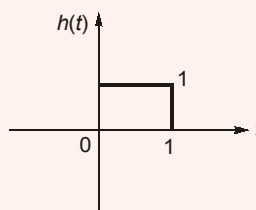

$z(t)$

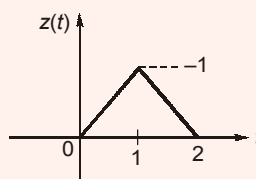
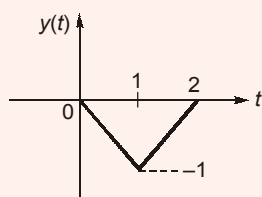


Case-2:

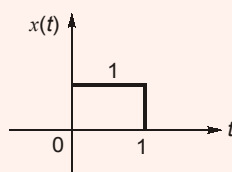

then,

$$y(t) = z(t)$$

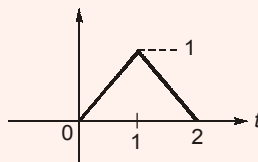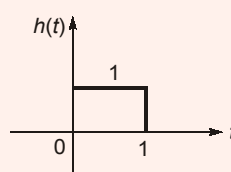

Thus,

$$z(t) \geq y(t), \text{ for all 't'}$$

End of Solution

Q.41 A signal $x(n)$ is given by $\left(\frac{1}{2}\right)^n u(n)$ where,

$$u(n) = \begin{cases} 1 & n \geq 0 \\ 0 & n < 0 \end{cases}$$

Z-transform $x(n-K)$ is $\frac{Z^{-K}}{1 - \frac{1}{2}Z^{-1}}$, then what will be ROC of $x(n-K)$

(a) $Z > \frac{1}{2}$

(b) $Z < 2$

(c) $Z > 2$

(d) $Z < \frac{1}{2}$

Ans. (a)

$$x(n) = \left(\frac{1}{2}\right)^n u(n), \text{ ROC of } x(n) : |z| > \frac{1}{2}$$

$$x(n-K) \xrightarrow{\text{Z-transform}} X(z) = \frac{Z^{-K}}{1 - \frac{1}{2}Z^{-1}}, \text{ ROC of } x(n-K) : |z| > \frac{1}{2}$$

For $x(n-K)$ ROC will be $|z| > \frac{1}{2}$.

End of Solution

Q.42 If x_A and x_R are average and rms values of signal $x(t) = x(t-T)$ respectively. y_A and y_R are average and rms value of signal $y(t) = Kx(t)$ respectively. K and T are independent of t .

(a) $y_A = Kx_A, y_R = Kx_R$

(b) $y_A \neq Kx_A, y_R = Kx_R$

(c) $y_A = Kx_A, y_R \neq Kx_R$

(d) $y_A \neq Kx_A, y_R \neq Kx_R$

Ans. (a)

Given that,

$$\Rightarrow \text{Average } x(t) = X_A, \quad \text{Rms } x(t) = X_R$$

$$\Rightarrow \text{Average } y(t) = Y_A, \quad \text{Rms } y(t) = Y_R$$

$$\Rightarrow x(t) = x(t-T)$$

$$\Rightarrow y(t) = Kx(t) \quad \dots(i)$$

$$\Rightarrow Y_A = KX_A$$

Since, Power $y(t) = |K|^2$ power $x(t)$

$$\Rightarrow \text{Rms } y^2(t) = |K|^2 \text{Rms } x^2(t)$$

$$\Rightarrow \text{Rms } y(t) = |K| \text{Rms } x(t)$$

$$\Rightarrow Y_R = |K| X_R$$

Assuming K as real and positive,

$$Y_R = K X_R$$

End of Solution

- Q.43** Which of the following statement is true about the two sided Laplace transform?
- (a) It always exists for a signal that may or may not have Fourier transform.
 - (b) It has no poles for any bounded signal that is non-zero only inside a finite time interval.
 - (c) If a signal can be expressed as a weighted sum of shifted one sided exponentials, then its Laplace transform will have no poles.
 - (d) The number of finite poles finite zeros must be equal.

Ans. (b)

End of Solution

- Q.44** A 50 Hz, power system network is operated under load of 100 MW. When the load is increases, the power input by the synchronous generator is increases by 10 MW and frequency of the rpm fall to 49.75 Hz. What will be the load at power system for the frequency falls to 49.25 Hz?

Ans. (130)


Assumed full load frequency is 50 Hz

$$\tan \theta = \frac{50 - 49.75}{110 - 100} = \frac{49.75 - 49.25}{(x - 110)}$$

$$\frac{0.25}{10} = \frac{0.5}{(x - 110)}$$


$$x - 110 = \frac{0.5 \times 10}{0.25}$$

$$x = 110 + 20 = 130 \text{ MW}$$

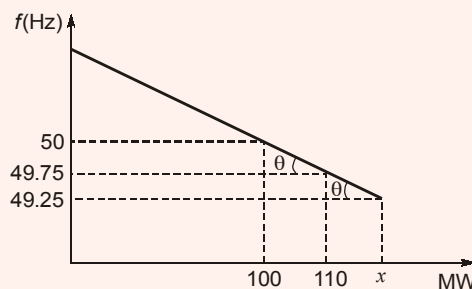

End of Solution

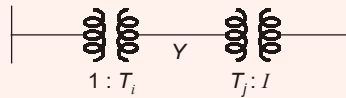
- Q.45** Find admittance matrix 2 bus is connected by 2 transformers having ratios $1 : T_i$ and $T_j : 1$ respectively and line having Y admittance.



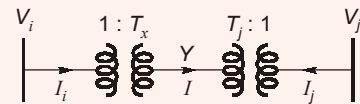- (a) $\begin{bmatrix} T_i^2 & -T_i T_j \\ -T_i T_j & T_j^2 \end{bmatrix}$ (b) $\begin{bmatrix} -T_i^2 & T_i T_j \\ T_i T_j & -T_j^2 \end{bmatrix}$
(c) $\begin{bmatrix} T_i T_j & -T_j^2 \\ -T_i^2 & T_i T_j \end{bmatrix}$ (d) $\begin{bmatrix} T_i T_j & -T_j^2 \\ -T_i^2 & T_i T_j \end{bmatrix}$

Ans. (a)

$$\begin{aligned} I &= Y(T_i V_i - V_j T_j) \\ I_i &= T_i I \\ &= T_i^2 Y V_i - T_i T_j Y V_j \\ I_j &= -T_j I \\ &= -T_j T_i Y V_i + T_j^2 Y V_j \\ \begin{bmatrix} I_i \\ I_j \end{bmatrix} &= \begin{bmatrix} T_i^2 Y & -T_i T_j Y \\ -T_i T_j Y & T_j^2 Y \end{bmatrix} \begin{bmatrix} V_i \\ V_j \end{bmatrix} \end{aligned}$$




End of Solution

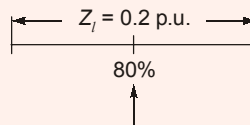- Q.46** A transmission line is being protected by distance protection. 80% of the line is being protected. The transfer reactance is 0.2 p.u. A solid 3- ϕ , fault occurred at the end of the transmission line. The minimum level of fault current to activate the relay
- (a) 6.25 (b) 5
(c) 1.25 (d) 3

Ans. (a)

$$I_f = \frac{1}{Z_{Th}} = \frac{1}{0.2} = 5 \text{ pu for 100\% of line}$$




Relay is operated for 80%

$$Z_f = 0.8 Z_l \Rightarrow 0.8 \times 0.2 = 0.16 \text{ p.u.}$$

For 80% of line,
$$I_f = \frac{1}{0.16} = 6.25 \text{ p.u.}$$

End of Solution

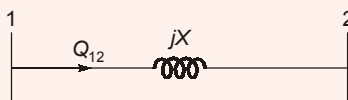- Q.47** Voltage at bus 1 = 1.1 p.u.
Voltage at bus 2 = 1 p.u.




Voltage at bus 2 is kept constant, Q_{12} is the sending reactive power from 1 to 2. On changing the bus 1 voltage, Q_{12} increases by 20%. Active power is zero in both the condition find the new value of bus 1 voltage.

Ans. (#)
A

End of Solution

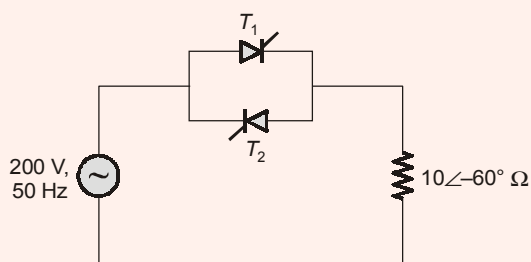- Q.48** In AC voltage controller shown below. Thyristor T_1 is fired at α and T_2 is fired at $180^\circ + \alpha$. To control the output power over range 0 to 2 kW. The minimum range of variation in α is



- (a) 0° to 60°
(b) 0° to 120°
(c) 60° to 120°
(d) 60° to 180°

Ans. (d)

End of Solution

- Q.49** A 1- ϕ , fully controlled rectifier is connected to highly inductive RL load with $R = 10 \Omega$ at 230 V, 50 Hz. The source inductance is 2.28 mH. If the firing angle $\alpha = 45^\circ$, then the overlapping angle will be

Ans. (4.25)

1- ϕ , SCR bridge rectifier

$$\alpha = 45^\circ, R = 10 \Omega$$

supply 230 V, 50 Hz

$$L_s = 2.28 \text{ mH}$$

$$\mu = ?$$

$$\Delta V_d = \frac{V_m}{\pi} [\cos \alpha - \cos(\alpha + \mu)] = 4f L_s I_0$$

$$V_0 = \frac{2V_m}{\pi} \cos \alpha - 4f L_s I_0$$

$$I_0 R = \frac{2V_m}{\pi} \cos \alpha - 4f L_s I_0$$

Find I_0

$$I_0 \text{ 10} = \frac{2.230\sqrt{2}}{\pi} \cdot \cos 45 - 4 \times 50 \times 2.28 \times 10^{-3} I_0$$

$$I_0(10 + 0.456) = 146.64$$

$$I_0 = \frac{146.49}{10.456} = 14.01 \text{ A}$$

$$\Delta V_{cd} = \frac{230\sqrt{2}}{\pi} [\cos 45 - \cos(45 + \mu)] = 4 \times 50 \times 2.28 \times 10^{-3} \times 14$$

$$= 6324$$


$$\cos 45^\circ - \cos(45^\circ + \mu) = 0.061$$

$$45 + \mu = 49.75$$

$$\therefore \mu = 4.25^\circ$$

End of Solution

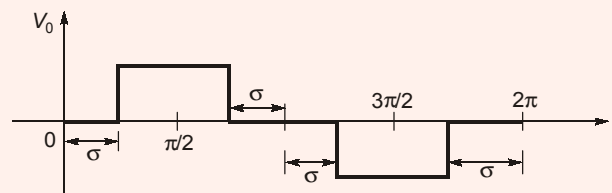Q.50 Value of σ adjusted so that 3rd harmonic is completely eliminated. Find the percentage magnitude of 5th harmonic w.r.t. fundamental component at this condition.



Ans. (20)


End of Solution

Q.51 A single-phase, 50 Hz full bridge rectifier with highly inductive RL load. The two most dominant frequency components will be

- (a) 50 Hz, 150 Hz (b) 50 Hz, 100 Hz
(c) 150 Hz, 250 Hz (d) 50 Hz, 0 Hz

Ans. (a)

1- ϕ full bridge rectifier,

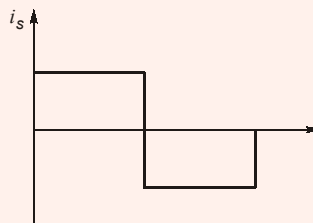


$$n = 1, 3, 5, \dots$$

$f = 50, 150, 250$ dominant


End of Solution

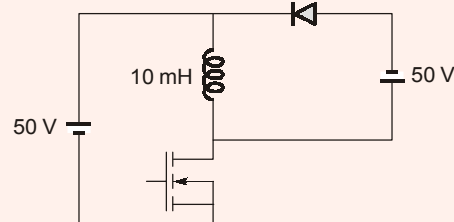- Q.52** A DC-DC converter shown below having switching frequency of 10 kHz with duty ratio 0.6. All the components are ideal and initial inductor current is zero. Energy stored in the inductor (in mJ) at the end of 10 switching cycles is



Ans. (5)

Buck boost converter

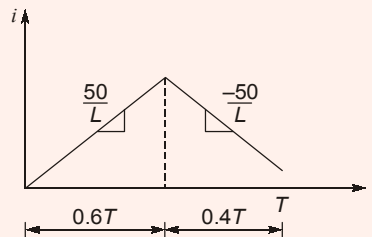

$D = 0.6 \rightarrow$ stores energy

$$D = \frac{T_{ON}}{T} = 0.6$$

$T_{ON} = 0.6T \rightarrow$ store energy

$T_{OFF} = 0.4T \rightarrow$ releasing energy

For one cycle: Rise in current for $0.2T$

For 10 cycles: Find rise in current $(0.2T) \times 10 = 2T$

$$i = \frac{50}{L}t$$

$$i = \frac{50}{L}(2T) = \frac{50 \times 2}{LP} = \frac{100}{10 \cdot 10^{-3} \times 10 \cdot 10^3} = 1A$$

$$\therefore \text{Energy stored} = \frac{1}{2}Li^2 = \frac{1}{2} \times (10 \cdot 10^{-3}) \cdot (1)^2 = 5 \text{ mJ}$$

End of Solution

UPPSC

Combined State Engineering Services Exam, 2019



MADE EASY
India's Best Institute for IES, GATE & PSUs

Assistant Engineer | Total Posts : 692

Classroom Course

Streams: CE, ME, EE

Commencing from 10th Feb, 2020 | Classes at Delhi and Lucknow

- 650 Hrs of comprehensive course.
- General Studies and Hindi covered.
- Exclusive study materials will be provided as per requirement of UPPSC.

Admission open

Postal Course

Streams: CE, ME, EE

Enrollment open

- Technical theory books with practice questions.
- Previous years' solved papers.
- Practice books (MCQ) for technical subjects.
- General Studies theory book with practice questions.
- Hindi book with practice questions.

Admission open

Live/Online Classes

Streams: CE, ME, EE

Commencing from 10th Feb, 2020

- Useful for those candidates who are not able to join classroom programme.
- 650 Hrs of quality classes at your doorstep.
- Flexibility to learn at your own pace.
- Physical study materials will be dispatched at your address.

Admission open

Test Series (Online/Offline)

Streams: CE, ME, EE

20 Tests | Commencing from 23rd Feb, 2020

- Quality questions with detailed solutions.
- Comprehensive performance analysis.
- Tests on standard and pattern as per UPPSC examination.


Admission open

Q.53 $R_T \rightarrow$ Thermistor

$$R_T = 2(1 + \alpha T)$$

Temperature rise = 150%

Find errors in the output voltage?

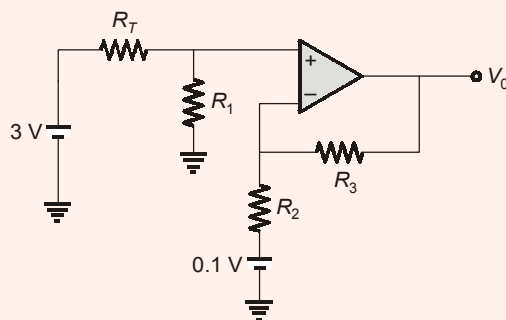


$$R_1 = 1 \text{ k}\Omega, \quad R_2 = 1.3 \text{ k}\Omega, \quad R_3 = 2.6 \text{ k}\Omega$$

Ans. ()

End of Solution

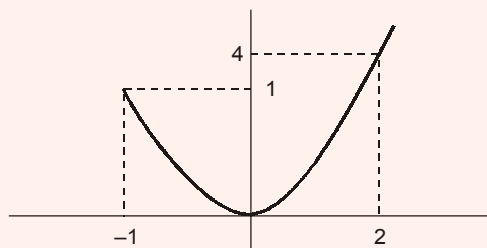Q.54 A vector function is given by $\vec{F} = y\hat{a}_x - x\hat{a}_y$. The line integral of the above function

$\int_C \vec{F} \cdot d\vec{l}$ along the curve C given by $y = x^2$ as shown below _____.



Ans. (-2.33)

$$\vec{F} = y\hat{a}_x - x\hat{a}_y$$

$$\vec{F} = y\vec{i} - x\vec{j}$$

$$\int_C \vec{F} \cdot d\vec{r} = \int_C F_1 dx + F_2 dy$$

$$y = x^2$$

$$dy = 2x dx$$

$$= \int x^2 dx - x \cdot 2x dx$$

$$= \int (x^2 - 2x^2) dx = \int_{-1}^2 -x^2 dx = \left(-\frac{x^3}{3} \right) \Big|_{-1}^2$$

$$= \frac{-8}{3} + \frac{1}{3} = \frac{-7}{3} = -2.33$$

End of Solution

Q.55 $\frac{dy}{dx} = 2x - y$, $y(0) = 1$. Find y at $x = \ln 2$

Ans. (0.886)

$$\frac{dy}{dx} = 2x - y; \quad y(0) = 1, y \text{ at } x = \ln 2$$

$$\frac{dy}{dx} + y = 2x$$

$$P = 1,$$

$$Q = 2x$$

$$I.F. = e^{\int P dx} = e^{\int 1 dx} = e^x$$

Solution, $y(I.F.) = \int Q(I.F.) dx$

$$ye^x = \int 2x \cdot e^x dx = 2(xe^x - e^x) + C$$

$$y = 2x - 2 + ce^{-x}$$

$$y(0) = 1$$

$$1 = 0 - 2 + C$$

$$C = 3$$

$$y = 2x - 2 + 3e^{-x}$$

\therefore

At $x = \ln 2$

$$y = 2(\ln 2) - 2 + 3e^{-\ln 2}$$

$$= 1.386 - 2 + \frac{3}{2} = 0.886$$

End of Solution

Q.56 Value of integral $\oint \frac{z^2+1}{z^2-2z}$ along the contour $|z| = 1$ is


- (a) πi (b) $-\pi i$
(c) $8\pi i$ (d) $-8\pi i$

Ans. (b)

$$\begin{aligned} \int_C \frac{z^2+1}{z^2-2z} dz \text{ where } C \text{ is } |z| = 1 \\ = \int \frac{z^2+1}{z(z-2)} dz \\ = \int \frac{z^2+1}{z} dz \end{aligned}$$

By integral formula,
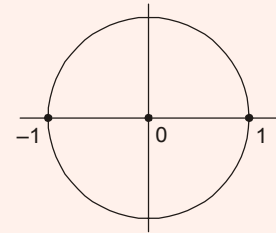
$$2\pi i f(0) \text{ where, } f(z) = \frac{z^2+1}{z-2} = 2\pi i \left(\frac{1}{-2} \right) = -\pi i$$



End of Solution

Q.57 The number of purely real elements in lower triangular representation of given 3×3 matrix obtained through given decomposition is

$$\begin{bmatrix} 2 & 3 & 3 \\ 3 & 1 & 2 \\ 3 & 6 & 5 \end{bmatrix} = \begin{bmatrix} a_{11} & 0 & 0 \\ a_{21} & a_{22} & 0 \\ a_{31} & a_{32} & a_{33} \end{bmatrix} \begin{bmatrix} a_{11} & 0 & 0 \\ a_{21} & a_{22} & 0 \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

Ans. (#)

$$\begin{bmatrix} 2 & 3 & 3 \\ 3 & 1 & 2 \\ 3 & 6 & 5 \end{bmatrix} = \begin{bmatrix} l_{11} & 0 & 0 \\ l_{21} & l_{22} & 0 \\ l_{31} & l_{32} & l_{33} \end{bmatrix} \begin{bmatrix} u_{11} & u_{12} & u_{13} \\ 0 & u_{22} & u_{23} \\ 0 & 0 & u_{33} \end{bmatrix}$$

$$\begin{bmatrix} 2 & 3 & 3 \\ 3 & 1 & 2 \\ 3 & 6 & 5 \end{bmatrix} = \begin{bmatrix} l_{11} & 0 & 0 \\ l_{21} & l_{22} & 0 \\ l_{31} & l_{32} & l_{33} \end{bmatrix} \begin{bmatrix} 1 & u_{12} & u_{13} \\ 0 & 1 & u_{23} \\ 0 & 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 2 & 3 & 3 \\ 3 & 1 & 2 \\ 3 & 6 & 5 \end{bmatrix} = \begin{bmatrix} l_{11} & l_{11}u_{12} & l_{11}u_{13} \\ l_{21} & l_{21}u_{12} + l_{22} & l_{21}u_{13} + l_{22}u_{23} \\ l_{31} & l_{31}u_{12} + l_{32} & l_{31}u_{13} + l_{32}u_{23} + l_{33} \end{bmatrix}$$

$$\begin{aligned} l_{11} &= 2 & l_{11}u_{12} &= 3 & l_{11}u_{13} &= 3 \\ & & 2u_{12} &= 3 & 2u_{13} &= 3 \\ l_{21} &= 3 & u_{12} &= \frac{3}{2} & u_{13} &= \frac{3}{2} \\ l_{31} &= 3 & & & & \end{aligned}$$

$$l_{21}u_{12} + l_{22} = 1$$

$$3\left(\frac{3}{2}\right) + l_{22} = 1$$

$$l_{21}l_{13} + l_{22}u_{23} = 2$$

$$u_{23} = \frac{2 - \frac{9}{2}}{\frac{-7}{2}} = \frac{5}{7}$$

$$u_{23} = \frac{5}{7}$$

$$l_{22} = 1 - \frac{9}{2} = \frac{-7}{2}$$

$$l_{22} = \frac{-7}{2}$$

$$l_{31}u_{12} + l_{32} = 6$$

$$(3)\left(\frac{3}{2}\right) + l_{32} = 6$$

$$l_{32} = 6 - \frac{9}{2} = \frac{3}{2}$$

$$l_{32} = \frac{3}{2}$$

$$l_{31}u_{13} + l_{32}u_{23} + l_{33} = 5$$

$$l_{33} = 5 - \frac{9}{2} - \frac{15}{14}$$

$$l_{33} = \frac{70 - 63 - 15}{14} = \frac{-8}{14} = \frac{-4}{7}$$

$$l_{33} = \frac{-4}{7}$$

End of Solution

Q.58 If $y = 3x^2 + 3x + 1$, for $x \in [-2, 0]$, find maximum and minimum value in the given range.

(a) 4 and 1

(b) 7 and $\frac{1}{4}$

(c) $\frac{1}{4}$ and 1

(d) -2 and $\frac{1}{-2}$

Ans. (b)

$$y = 3x^2 + 3x + 1 \quad \text{in } [-2, 0]$$

$$\frac{\partial y}{\partial x} = 6x + 3,$$

$$\frac{\partial^2 y}{\partial x^2} = 6$$

$$\frac{dy}{dx} = 0$$

$$6x + 3 = 0$$

$$x = -\frac{1}{2}$$

$$\frac{d^2y}{dx^2} = 6 > 0 \text{ minimum}$$

Maximum value of y in $[-2, 0]$ is maximum $\{f(-2), f(0)\}$

$$\max\{7, 1\} = 7$$

Minimum value of y in $[-2, 0]$

$$\min \left\{ \begin{matrix} f(-2) & f(0) & f\left(-\frac{1}{2}\right) \\ \downarrow & \downarrow & \downarrow \\ 7 & 1 & \frac{1}{4} \end{matrix} \right\} = \frac{1}{4}$$

Maximum value 7, minimum value $\frac{1}{4}$.

End of Solution

Q.59 Which of the following is true?

(a) $\frac{1}{\pi} \int_0^\pi \sin m\omega t \sin n\omega t = 0 \quad m \neq n$

(b) $\frac{1}{\pi} \int_{-\pi}^\pi \sin p\omega t \sin q\omega t = 0$

(c) $\frac{1}{2\pi} \int_0^\pi \cos p\omega t \cos q\omega t = 0$

(d) $\frac{1}{2\pi} \int_{-\pi}^\pi \sin p\omega t \cos q\omega t = 0$

Ans. (d)

End of Solution

